



DRAW YOUR DIAGRAM ON THIS PAGE

EXAMINATION FOR THE ISSUE OF A LICENCE TO ACT AS WIREMAN - LIC'A
Practical Test 2013 Time Allowed: 1 Hr

NAME & SURNAME _____ INDEX NO. _____
(in Block letters)

- 1a) Using the proper symbols plot on the plan provided the required electrical fittings as to comprise a complete and safe installation.
- b) Using a single-line diagram show how the circuits are to be distributed.
- c) If the installation is to be made up of:
 - i. Three ring-circuits.
 - ii. Two Lighting circuits.
 - iii. One water heater circuit.
 - iv. One cooker-circuit.

Draw a diagram showing the consumer unit required according to Legal Notice 225 of 2010 & IEE regulations.

END OF PAPER