

# EXAMINATION FOR THE ISSUE OF AUTHORISATION 'B' - LICENCE 'B'

Practical Test

September 2015

Time Allowed: 1 Hr

NAME & SURNAME \_\_\_\_\_ (in Block letters)

INDEX NO \_\_\_\_\_

---

WRITE BELOW THIS LINE

---

The electrical load of a small factory consists of the following components:

- a. 1 x 60 KW three phase electrode boiler having an efficiency of 85 per cent and unity power factor.
- b. 2 x 8 KW three phase motors, 0.8 power factor and 85 per cent efficiency.
- c. 60 lighting points.
- d. 10 KW of discharge lighting, power factor 0.85.
- e. 10 x 32A ring circuits.
- f. 4 x 3 KW instantaneous type water heaters.

Assuming a three-phase 400/230 Volts supply,

- i. Draw a single line diagram of the main switch-board indicating the current rating of each switch and type of protection.
- ii. Calculate the total current demand.
- iii. Taking a diversity factor of 70 per cent and allowing for future expansion calculate a suitable size of switch-board and main circuit breaker for the installation.

Show all calculations.

WRITE BELOW THIS LINE

---

WRITE BELOW THIS LINE

---