

Scanned

6. A storage battery is made up of 50 cells in series. The battery is to be charged at a constant rate of 40 amperes from a 220 volt supply.

The e.m.f. per cell before the start of charge is 2.2 volts and at the end of the charge the e.m.f. rises to 2.5 volts per cell.

The internal resistance of each cell is 0.006 ohm.

What resistance must be placed in series with the battery to keep the charging current constant at 40 amperes?

- a) At the start of charging. (6 marks)
- b) At the end of charging. (6 marks)
- c) What percentage of the total energy developed is actually used to charge the battery? (6 marks)
- d) Draw a diagram of the arrangement. (2 marks)

**EXAMINATION: AUTHORIZATION B**

February 2017

Paper I (Theory)

Time Allowed: 3 Hrs

**END OF PAPER**

WRITE ALL YOUR WORK IN THE ANSWER BOOK PROVIDED.  
EVERY ANSWER SHOULD INCLUDE ALL WORKINGS, NECESSARY  
DIAGRAMS AND FORMULAE.

START EACH ANSWER ON A FRESH PAGE.

Answer any FIVE Questions

1. A coil of inductance  $162.34 \text{ mH}$  and a resistance  $50 \Omega$  is connected in parallel with a  $30 \mu\text{F}$  capacitor, across a  $230 \text{ V}$ ,  $50 \text{ Hz}$  supply. Sketch the circuit and phasor diagrams and calculate:
  - a) The current in the coil and its phase angle. (6 marks)
  - b) The current in the capacitor and its phase angle. (5 marks)
  - c) The supply current and its phase angle. (5 marks)
  - d) The circuit impedance. (2 marks)
  - e) The power consumed. (2 marks)
  
2. a) Define Kirchoff's Laws i.e. current law and voltage law. (4 marks)
  
- b) Refer to Figure 1:  
Re draw Figure 1 and assume that the current flows from the positive terminals of the batteries. Label ALL branch currents flowing. (4 marks)
  
- c) Use Kirchoff's laws to determine the currents flowing in each branch of the network. (12 marks)

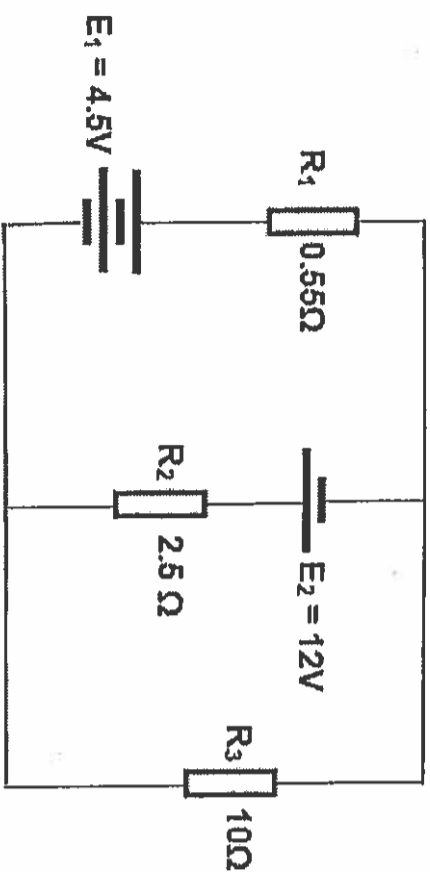


Figure 1

3. a) Deduce the E.m.f. equation for a transformer (6 marks)
  
- b) Explain why the ferrous magnetic circuits subject to alternating magnetism are usually laminated and give examples of typical core construction for three phase transformers. (4 marks)
  
- c) A  $40 \text{ kVA}$  has a core loss of  $450 \text{ W}$  and full-load copper losses of  $850 \text{ W}$ . If the power factor of the load is  $0.8$ , calculate:
  - i. The full load efficiency (5 marks)
  - ii. The maximum efficiency assuming the power factor of the load remains  $0.8$  (5 marks)
  
4. a) State and briefly describe four types of losses which occur in a DC machine (5 marks)
  
- b) Draw the Torque / Speed characteristic for a series motor and a shunt motor (2 marks)
  
- c) A series motor runs at  $800 \text{ rev / min}$  when the supply voltage is  $400 \text{ V DC}$  and draws a current of  $25 \text{ A}$  from the supply. The armature resistance is  $0.4 \Omega$  and the series field resistance is  $0.2 \Omega$ . Determine the resistance to be connected in series with the motor to reduce the speed to  $600 \text{ rev / min}$  with the motor still continuing to draw a current of  $25 \text{ A}$  from the supply. (13 marks)
  
5. The power input to a  $250 \text{ h.p.}$ ,  $1100 \text{ volt}$ , three-phase motor running at full load is measured by two watt-meters which read,  $145 \text{ kW}$  and  $62 \text{ kW}$  respectively. Calculate:
  - a) the input power. (4 marks)
  - b) the p.f. (5 marks)
  - c) the line current. (5 marks)
  - d) the efficiency. (4 marks)
  - e) Draw a diagram showing how the watt-meters are connected to the motor. (2 marks)