

**WRITE ALL YOUR WORK IN THE ANSWER BOOK PROVIDED. EVERY ANSWER SHOULD INCLUDE ALL WORKINGS, NECESSARY DIAGRAMS AND FORMULAE.**

**START EACH ANSWER ON A FRESH PAGE.**

Choose any FIVE questions.

1. A 3m x 1m kitchen working top for food preparation is to have lighting design fixed 60cm above that would satisfy minimum 538 lux.
  - i. Describe and define Utilisation Factor (UF) in lighting design. (3 marks)
  - ii. Name two factors affecting the utilisation factor. (2 marks)
  - iii. Describe Maintenance Factor (MF) in lighting design. (5 marks)
  - iv. Describe and define the space height ratio. (2 marks)

Using the Lumen Method and considering 5050 LED light with average 19 lumens, UF of 0.6 and MF 0.7. Calculate:

- v. how many LEDs are required. (3 marks)
- vi. the minimum spacing between each LED, including:
  - (a) numbers in rows,
  - (b) LEDs per row,
  - (c) axial spacing and
  - (d) transverse spacing. (5 marks)

2. (a) Name two methods for charging secondary batteries. For each method briefly explain how the batteries are charged. (8 marks)

- (b) Twelve cells each of emf 2.2V and internal resistance of 0.15 Ohm are arranged in three parallel rows. The whole cells arrangement forms a battery which is supplying a load of resistance 8 Ohms. Calculate,
  - i. The load current, (4 marks)
  - ii. The battery terminal voltage (4 marks)
  - iii. The load power supplied by the battery. (4 marks)

3. (a) State Ohm's Law as applied to a direct current (DC) circuit (3 marks)

- (b) A circuit consisting of three resistors of resistances 8 Ohms, 7 Ohms and 4 Ohms connected in parallel, in series with a fourth resistor of resistance 3.5 Ohms across a 20 Volts direct current (DC) supply.

Draw the circuit showing the resistors combination. (3 marks)

(c) Calculate:

- i. The total resistance (2 marks)
- ii. The total current (2 marks)
- iii. The voltage drop across the 3.5 Ohms resistor (2 marks)
- iv. The current through the 8 Ohms resistor (2 marks)
- v. The total power (2 marks)
- vi. The power dissipated by the 4 Ohms resistor (2 marks)
- vii. The power dissipated by the 3.5 Ohms resistor (2 marks)

4. A test on an electric kettle gave the following results:

Volume of water	0.001 m <sup>3</sup>
Supply voltage	235 Volts
Current	6.2 Amps
Initial temperature	18° C
Final temperature	100° C
Time taken	330 seconds

Taking that: mass of 1m<sup>3</sup> of water = 1000 kg = 1000 litres  
 temperature coefficient of water = 4187 Joules  
 1 kWh = 3.6 x 10<sup>6</sup> Joules

Determine the efficiency of the kettle.

(20 marks)

5. A resistor of 200 Ohms and a capacitor of unknown value are connected in series to a 240 Volts supply at a frequency of 50 Hz. A current of 0.85 Amperes flows in the circuit.

- i. Draw the circuit diagram. (4 marks)
- ii. Find the impedance of the circuit. (6 marks)
- iii. Calculate the value of the capacitor in microfarads. (10 marks)

6. A 95% efficient 50 litre water electric boiler is to raise the temperature of water by 40°C in 30 minutes. Calculate:

- i. The heat energy required by the water (5 marks)
- ii. The electrical energy input to the heater (5 marks)
- iii. The average electric power supplied, and (5 marks)
- iv. The cost of energy at €0.11/kWh. (5 marks)

Neglecting the heat absorbed by the surroundings.

Specific heat capacity of water is 4.186 J/g°C.

**END OF PAPER**

**EXAMINATION: AUTHORISATION A**

Paper I (Theory)

Time Allowed - 3Hrs

February 2018